

# Andhra Pradesh State Council of Higher Education

## Notations :

- 1.Options shown in green color and with ✓ icon are correct.
- 2.Options shown in red color and with ✘ icon are incorrect.

<b>Question Paper Name :</b>	Electronics and Communication Engineering 29th April 2026 Shift 1
<b>Subject Name :</b>	Electronics and Communication Engineering
<b>Creation Date :</b>	2026-04-29 13:04:42
<b>Duration :</b>	120
<b>Number of Questions :</b>	120
<b>Total Marks :</b>	120
<b>Display Marks:</b>	No
<b>Change Font Color :</b>	No
<b>Change Background Color :</b>	No
<b>Change Theme :</b>	No
<b>Help Button :</b>	No
<b>Show Reports :</b>	No
<b>Show Progress Bar :</b>	No

## Electronics and Communication Engineering

<b>Group Number :</b>	1
<b>Group Id :</b>	75207658
<b>Group Maximum Duration :</b>	0
<b>Group Minimum Duration :</b>	120
<b>Show Attended Group? :</b>	No
<b>Edit Attended Group? :</b>	No
<b>Break time :</b>	0

**Group Marks :**

120

## **Electronics and Communication Engineering**

<b>Section Id :</b>	75207658
<b>Section Number :</b>	1
<b>Section type :</b>	Online
<b>Mandatory or Optional :</b>	Mandatory
<b>Number of Questions :</b>	120
<b>Number of Questions to be attempted :</b>	120
<b>Section Marks :</b>	120
<b>Section Negative Marks :</b>	0
<b>Maximum Instruction Time :</b>	0
<b>Sub-Section Number :</b>	1
<b>Sub-Section Id :</b>	75207658
<b>Question Shuffling Allowed :</b>	Yes
<b>Is Section Default? :</b>	No

**Question Number : 1 Question Id : 7520766841 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

The number of nodes in a graph having 5 branches and 2 independent loops is

**Options :**


1. ✘ 3
2. ✔ 4
3. ✘ 5

4. ✘ 6

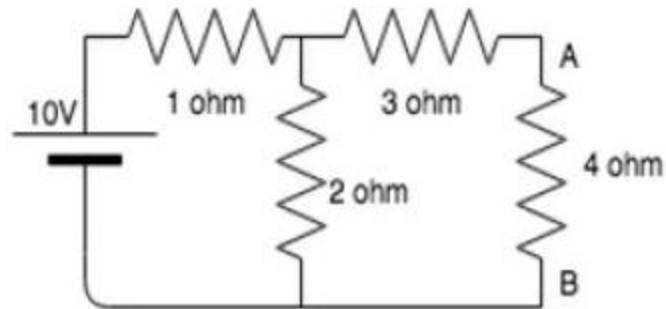Question Number : 2 Question Id : 7520766842 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

For the given circuit, the values of  $R_{th}$  across the terminal AB and  $V_{th}$  are \_\_\_ and \_\_\_, respectively.



Options :

- 1. ✘ 4.34  $\Omega$ , 5.54 V
- 2. ✘ 3.67  $\Omega$ , 3.33 V
- 3. ✘ 3.43  $\Omega$ , 6.67 V
- 4. ✔ 3.67  $\Omega$ , 6.67 V

Question Number : 3 Question Id : 7520766843 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If a Delta circuit has branches  $R_{ab} = 10 \Omega$ ,  $R_{bc} = 20 \Omega$ , and  $R_{ca} = 30 \Omega$ , what is the equivalent Wye resistor  $R_a$  connected to node?

Options :

1. ✘ 10  $\Omega$
2. ✘ 20  $\Omega$
3. ✘ 30  $\Omega$
4. ✔ 5  $\Omega$

Question Number : 4 Question Id : 7520766844 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In sinusoidal steady-state analysis, which of the following best describes the use of phasors?

Options :

1. ✔ Phasors are used to simplify time-domain analysis of RLC circuits by representing sinusoidal signals as complex numbers
2. ✘ Phasors are only used for DC analysis

3. ✘ Phasors convert differential equations into algebraic equations in the time domain

4. ✘ Phasors are used to compute the time derivative of voltage or current

**Question Number : 5 Question Id : 7520766845 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

What does the Laplace transform do the differential equation of an RLC circuit?

**Options :**

1. ✘ It simplifies the equation by transforming it from the frequency domain to the time domain

2. ✘ It retains the differential equation as it is

3. ✔ It converts the circuit parameters into phasor form

4. ✘ It converts a time-domain differential equation into an algebraic equation in the s-domain

**Question Number : 6 Question Id : 7520766846 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

For a symmetrical two-port network, which of the following is NOT necessarily true?

Options :

1. ✘  $z_{11} = z_{22}$

2. ✘  $y_{11} = y_{22}$

3. ✘  $A = D$

4. ✔  $h_{12} = h_{21}$

Question Number : 7 Question Id : 7520766847 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following best describes the band structure of intrinsic silicon?

Options :

1. ✘ Single energy band

2. ✘ Completely overlapping conduction and valance bands

3. ✔ A wide band gap between the conduction and the valance bands

4. ✘ No conduction band

Question Number : 8 Question Id : 7520766848 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

The primary characteristic of a tunnel diode is its \_\_\_\_.

Options :

1. ✘ very high forward resistance
2. ✔ negative resistance
3. ✘ low breakdown resistance
4. ✘ high capacitance

Question Number : 9 Question Id : 7520766849 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

At very high electric fields in silicon, the drift velocity of electrons becomes independent of the electric field. This phenomenon is known as:

Options :

1. ✓ Velocity Saturation
2. ✘ Avalanche Breakdown
3. ✘ Negative Differential Resistance
4. ✘ Mobility Enhancement

**Question Number : 10 Question Id : 7520766850 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

In an n-channel JFET, if the gate voltage is made more negative than the pinch-off voltage, what happens to the drain current?

**Options :**

1. ✘ Drain current increases linearly
2. ✘ Drain current saturates
3. ✓ Drain current drops to near zero

4. ✘ Drain current reverses direction

Question Number : 11 Question Id : 7520766851 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

Which of the following is a characteristic of the MOS capacitor?

Options :

1. ✘ The capacitance is zero when there is no applied voltage

2. ✔ The capacitance increases with increasing voltage applied to the gate

3. ✘ The capacitance is independent of the gate voltage

4. ✘ The MOS capacitor can only store holes

Question Number : 12 Question Id : 7520766852 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

What distinguishes the light emitted by a LASER diode from an LED?

Options :

1. ✘ LED light is monochromatic

2. ✓ LASER light is coherent
3. ✗ LED light is directional
4. ✗ LASER light results from spontaneous emission

**Question Number : 13 Question Id : 7520766853 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

In silicon IC fabrication, 'Dry Oxidation' is generally preferred over 'Wet Oxidation' for growing:

**Options :**

1. ✗ Thick field oxides
2. ✓ Gate oxides
3. ✗ Isolation layers
4. ✗ Passivation layers

**Question Number : 14 Question Id : 7520766854 Question Type : MCQ**

Correct Marks : 1 Wrong Marks : 0

In a MOSFET small-signal model, if the drain current is doubled while maintaining the same device dimensions, the trans-conductance will:

Options :

1. ✘ Remain the same
2. ✘ Increase by a factor of 2
3. ✔ Increase by a factor of  $\sqrt{2}$
4. ✘ Decrease by a factor of  $\sqrt{2}$

Question Number : 15 Question Id : 7520766855 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A positive clamper circuit with a 10V DC source is fed with a 20V p-p sinusoidal input.

What is the minimum DC voltage level at the output?

Options :

1. ✘ 0 V
2. ✔ 10 V

3. ✘ 20 V

4. ✘ -10 V

**Question Number : 16 Question Id : 7520766856 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

A negative feedback amplifier has an open-loop gain of 100 and a feedback factor  $\beta = 0.09$ . If the open-loop gain changes by 10% due to aging, what is the percentage change in the closed-loop gain of the amplifier?

**Options :**

1. ✔ 1 %

2. ✘ 10 %

3. ✘ 0.1 %

4. ✘ 0.9 %

**Question Number : 17 Question Id : 7520766857 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

In an op-amp, which of the following best describes the 'virtual short' concept?

Options :

1. ✘ The op-amp behaves like a short circuit in feedback configuration
2. ✘ The op-amp input terminals are shorted together for operation
3. ✘ The output voltage of the op-amp is always zero
4. ✔ The voltage difference between the inverting and non-inverting inputs is close to zero in an ideal op-amp

Question Number : 18 Question Id : 7520766858 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A two-stage RC-coupled amplifier has stage-1 lower cutoff frequency  $f_{L1} = 100$  Hz and stage-2 lower cutoff frequency  $f_{L2} = 1$  kHz. The overall lower cutoff frequency of the amplifier is approximately:

Options :

1. ✘ 50 Hz

- 2. ✘ 100 Hz
- 3. ✘ 500 Hz
- 4. ✔ 1 kHz

**Question Number : 19 Question Id : 7520766859 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

Which of the following is a common application of a 555 timer in monostable mode?

**Options :**

- 1. ✘ To generate a constant output signal
- 2. ✔ To generate a fixed pulse with output signal
- 3. ✘ To oscillate continuously
- 4. ✘ To provide a frequency response

**Question Number : 20 Question Id : 7520766860 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

A full-wave rectifier has a load resistor of  $1\text{ k}\Omega$  and a capacitor of  $100\text{ }\mu\text{F}$ . Doubling the load resistor will \_\_\_\_\_.

Options :

1. ✘ double ripple voltage
2. ✔ halve ripple voltage
3. ✘ no change
4. ✘ quadruple ripple voltage

Question Number : 21 Question Id : 7520766861 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The minimal SOP expression for a 3-variable function having  $m$  in terms of

$\sum m(1, 3, 5, 7)$  is

Options :

1. ✔  $C$
2. ✘  $A+C$

3. ✘  $B$

4. ✘  $AB+C$

**Question Number : 22 Question Id : 7520766862 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

The logic family which is least affected by temperature variations, is

**Options :**

1. ✘ DTL

2. ✘ TTL

3. ✔ CMOS

4. ✘ ECL

**Question Number : 23 Question Id : 7520766863 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

In a positive edge-triggered  $JK$  flip-flop, the  $J$  input is connected to  $\bar{Q}$  (inverted output) and the  $K$  input is connected to  $Q$  (normal output). If the flip-flop is initially in the RESET state ( $Q=0$ ,  $\bar{Q}=1$ ) and is subjected to 4 consecutive positive clock pulses, what will be the final state of  $Q$ ?

Options :

1. ✘ 1
2. ✘ 0101 (oscillates)
3. ✔ 0
4. ✘ Indeterminate

Question Number : 24 Question Id : 7520766864 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If a sample and hold circuit is not used with an ADC, the result may be \_\_\_\_\_.

Options :

1. ✘ more accurate

2. ✘ constant
3. ✘ digitalized faster
4. ✔ erroneous due to changing input

**Question Number : 25 Question Id : 7520766865 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

A ring counter (with 4 flip-flops) has how many unique states?

**Options :**

1. ✘ 2
2. ✔ 4
3. ✘ 8
4. ✘ 16

**Question Number : 26 Question Id : 7520766866 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Signal distortionless transmission through an LTI system requires:

Options :

1. ✘ Constant magnitude response only
2. ✘ Linear phase only
3. ✔ Constant magnitude and linear phase
4. ✘ Zero group delay

Question Number : 27 Question Id : 7520766867 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The frequency response magnitude of a DT-LTI system tends to infinity when

Options :

1. ✘ Input is zero
2. ✔ Poles lie on the unit circle

3. ✘ Zeros lie on the unit circle

4. ✘ System is causal

**Question Number : 28 Question Id : 7520766868 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

What is the primary difference between CTFT and DTFT?

**Options :**

1. ✘ CTFT is periodic and DTFT is non-periodic

2. ✘ CTFT transforms a discrete-time signal and DTFT transforms a continuous-time signal

3. ✔ CTFT is non-periodic and DTFT is periodic

4. ✘ CTFT is defined for periodic signals and DTFT is for non-periodic signals

**Question Number : 29 Question Id : 7520766869 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

In a causal and stable LTI system, the impulse response  $h(t)$  must satisfy which condition ?

Options :

1. ✘  $h(t)$  is always positive
2. ✘  $h(t)$  is periodic
3. ✔  $h(t)$  must be absolutely integrable
4. ✘  $h(t)$  must be bounded

Question Number : 30 Question Id : 7520766870 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

What is the Fourier Transform of a Gaussian function  $e^{-t^2}$  ?

Options :

1. ✘ A delta function
2. ✘ A sinc function

3. ✓ Another Gaussian function

4. ✘ An exponential function

Question Number : 31 Question Id : 7520766871 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In FFT computation, reducing complexity from  $O(N^2)$  to  $O(N \log N)$  relies fundamentally on \_\_\_\_\_.

Options :

1. ✘ periodicity of time-domain signal

2. ✓ symmetry and periodicity of twiddle factors

3. ✘ linearity of DFT

4. ✘ convolution theorem

Question Number : 32 Question Id : 7520766872 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If the impulse response of a discrete-time LTI system is finite in length, which property is always guaranteed?

Options :

1. ✘ Causality
2. ✔ Stability
3. ✘ Linearity
4. ✘ Time invariance

Question Number : 33 Question Id : 7520766873 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

For a discrete-time periodic signal with period  $N$ , how many distinct Fourier coefficients exist?

Options :

1. ✘ Infinite
2. ✘  $N/2$

3. ✓  $N$

4. ✗  $2N$

Question Number : 34 Question Id : 7520766874 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The open loop transfer function of a unity feedback system is  $G(s) = \frac{10}{s(s+2)}$ ,

what is the steady state error for a unit step input?

Options :

1. ✗ Infinite

2. ✓ 0

3. ✗ 0.1

4. ✗ 0.2

Question Number : 35 Question Id : 7520766875 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A second order system has  $\omega_n = 4\text{rad/sec}$  and  $\zeta = 0.5$ . What is the damped natural frequency  $\omega_d$ ?

Options :

1. ✘ 4
2. ✘ 2
3. ✘ 1.73
4. ✔ 3.46

Question Number : 36 Question Id : 7520766876 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The characteristic equation of a system is  $s^3 + 3s^2 + 3s + 1 = 0$ . How many poles lie in the right half plane?

Options :

1. ✔ 0
2. ✘ 1

3. ✘ 2

4. ✘ 3

**Question Number : 37 Question Id : 7520766877 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

If the open-loop transfer function  $G(s)H(s)$  has one pole in the right-half of the  $s$ -plane, for the closed-loop system to be stable, the Nyquist plot must encircle the  $(-1, j0)$  point \_\_\_\_\_.

**Options :**

1. ✘ once in the clockwise direction

2. ✘ twice in the counter-clockwise direction

3. ✔ once in the counter-clockwise direction

4. ✘ zero times

**Question Number : 38 Question Id : 7520766878 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

A phase-lead compensator is primarily used to \_\_\_\_\_.

Options :

1. ✘ decrease the steady-state error
2. ✔ increase the damping and improve transient response
3. ✘ reduce the bandwidth of the system
4. ✘ increase the rise time

Question Number : 39 Question Id : 7520766879 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which part of a PID controller is specifically responsible for eliminating the steady-state error?

Options :

1. ✘ Proportional term
2. ✘ Feedforward term

3. ✘ Derivative term

4. ✔ Integral term

Question Number : 40 Question Id : 7520766880 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

For the state equation  $\dot{x} = 3x$ , the system is \_\_\_\_\_.

Options :

1. ✘ stable

2. ✘ marginally stable

3. ✔ unstable

4. ✘ oscillatory

Question Number : 41 Question Id : 7520766881 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Gain cross over frequency is the frequency at which \_\_\_\_\_.

Options :

1. ✘ Phase is zero
2. ✔ Magnitude is 0 dB
3. ✘ Phase is  $-180^\circ$
4. ✘ Gain is maximum

Question Number : 42 Question Id : 7520766882 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

What is the primary advantage of using a super-heterodyne receiver?

Options :

1. ✘ Simplicity in construction
2. ✘ High frequency response
3. ✔ Improved signal selectivity and sensitivity

Direct conversion of the received signal

4. ✘

Question Number : 43 Question Id : 7520766883 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following digital modulation schemes has the lowest probability of error at a given SNR?

Options :

1. ✘ ASK

2. ✘ FSK

3. ✔ PSK

4. ✘ DPSK

Question Number : 44 Question Id : 7520766884 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following is a salient feature of GSM \_\_\_\_\_.

Options :

1. ✘ frequency modulation for voice transmission
2. ✔ digital communication with TDMA and FDMA
3. ✘ analog communication with digital encoding
4. ✘ use of Satellite communication for signal transmission

Question Number : 45 Question Id : 7520766885 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a coherent BPSK modulation scheme, if the input bit rate is doubled while keeping the symbol energy as constant, what is the effect on the transmission bandwidth ( $BW$ ) and the probability of bit error ( $Pe$ )?

Options :

1. ✘  $BW$  doubles,  $Pe$  increases
2. ✔  $BW$  doubles,  $Pe$  remains same
3. ✘  $BW$  remains same,  $Pe$  increases

$BW$  doubles,  $P_e$  decreases

4. ✘

Question Number : 46 Question Id : 7520766886 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A Gaussian noise channel has a bandwidth of 4 kHz and a signal-to-noise power ratio (SNR) of 15. According to the Shannon-Hartley theorem, what is the maximum capacity of this channel?

Options :

1. ✘ 32 kbps

2. ✔ 16 kbps

3. ✘ 60 kbps

4. ✘ 64 kbps

Question Number : 47 Question Id : 7520766887 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The total average power of a signal equals:

Options :

1. ✘ Peak value of PSD
2. ✔ Integral of PSD over all frequencies
3. ✘ Fourier transform of PSD
4. ✘ Autocorrelation at infinity

Question Number : 48 Question Id : 7520766888 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

For a WSS random process, the autocorrelation  $R_x(\tau)$  as  $\tau \rightarrow \infty$  approaches:

Options :

1. ✘ Zero always
2. ✘ Mean square value
3. ✔ Square of the mean
4. ✘ Signal power

Question Number : 49 Question Id : 7520766889 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The skin depth in a conductor is:

Options :

1. ✘ Inversely proportional to conductivity
2. ✘ Directly proportional to square root of conductivity
3. ✔ Inversely proportional to square root of conductivity
4. ✘ Independent of material properties

Question Number : 50 Question Id : 7520766890 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following statements is NOT true about Maxwell's equations in differential form?

Options :

1. ✘ Gauss's Law states that the electric flux density is proportional to the charge density.

2. ✘ Faraday's Law implies that a time-varying magnetic field produces an electric field.
3. ✘ Ampère's Law with Maxwell's correction shows that a time-varying electric field produces a magnetic field.
4. ✔ Gauss's Law for magnetism states that the magnetic flux density has a net source.

**Question Number : 51 Question Id : 7520766891 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

The radiation pattern of a dipole antenna is characterized by,

**Options :**

1. ✘ A constant radiation intensity in all directions
2. ✔ A doughnut-shaped distribution with maximum radiation perpendicular to the axis
3. ✘ Maximum radiation along the axis of the dipole

A uniform radiation pattern in the far field

4. ✘

**Question Number : 52 Question Id : 7520766892 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

The Poynting vector in electromagnetic theory represents,

**Options :**

The electric field strength at a point

1. ✘

The rate at which energy is transported by the electromagnetic wave

2. ✔

The potential energy in the electric field

3. ✘

The time-averaged power dissipated in a resistor

4. ✘

**Question Number : 53 Question Id : 7520766893 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**


Which of the following is the primary condition that must be satisfied at the boundary of a perfect electric conductor (PEC) for an electromagnetic wave?

**Options :**

1. ✘ The tangential component of the magnetic field is zero
2. ✔ The tangential component of the electric field is zero
3. ✘ The normal component of the electric field is zero
4. ✘ The normal component of the magnetic field is zero

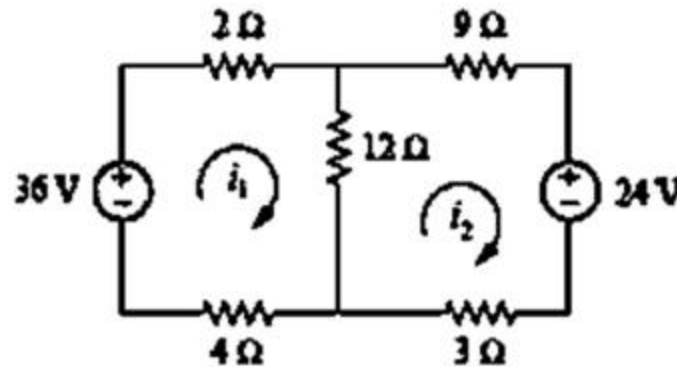Question Number : 54 Question Id : 7520766894 Question Type : MCQ  
 Correct Marks : 1 Wrong Marks : 0

Find current  $i_2$  in the shown network



Options :

1. ✔ 0A

2. ✘ 3A

3. ✘ 1A

4. ✘ 2A

**Question Number : 55 Question Id : 7520766895 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

For every tree there will be \_\_\_\_\_ number of cut set matrices.

**Options :**

1. ✔ 1


2. ✘ 2

3. ✘ 3

4. ✘ 4

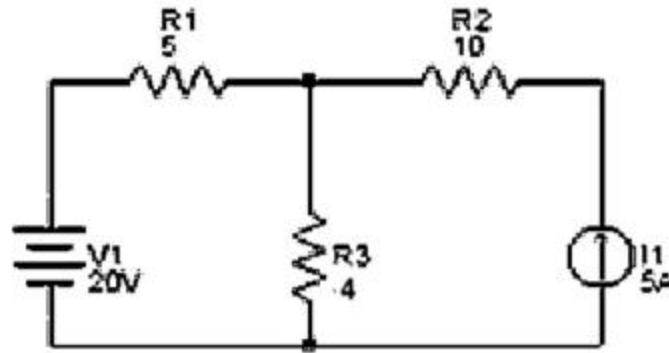**Question Number : 56 Question Id : 7520766896 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

In the circuit shown, find the current through  $4\Omega$  resistor using Superposition theorem.




Options :

1. ✘ 4
2. ✔ 5
3. ✘ 6
4. ✘ 7

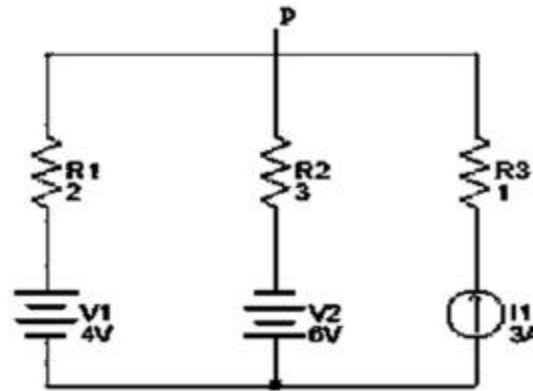Question Number : 57 Question Id : 7520766897 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

Find the voltage at node P, shown in the figure.



Options :

1. ✘ 9V
2. ✔ 3.6 V
3. ✘ 10V
4. ✘ 4.3V

Question Number : 58 Question Id : 7520766898 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In an R-C circuit, when the switch is closed, the response \_\_\_\_\_.

Options :

1. ✘ do not vary with time

2. ✓ decays with time
3. ✘ rises with time
4. ✘ first increases and then decreases

**Question Number : 59 Question Id : 7520766899 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

What type of semiconductor is used in LED ?

**Options :**

1. ✘ Intrinsic semiconductor
2. ✓ Compound semiconductor
3. ✘ Degenerated semiconductor
4. ✘ Compensated semiconductor

**Question Number : 60 Question Id : 7520766900 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

The voltage equivalent of temperature ( $V_T$ ) in a  $p-n$  junctions is given by

Options :

1. ✘ T/1000 volts
2. ✘ T/300 volts
3. ✘ T/1600 volts
4. ✔ T/11600 volts

Question Number : 61 Question Id : 7520766901 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The application of a CC configured transistor is\_\_\_\_\_.

Options :

1. ✘ voltage multiplier
2. ✘ level shifter
3. ✘ rectification

4. ✓ impedance matching

**Question Number : 62 Question Id : 7520766902 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

What is the behaviour of a PIN diode under reverse bias?

**Options :**

1. ✗ It conducts high current.
2. ✗ It acts as a variable resistor.
3. ✓ It acts as a variable capacitor.
4. ✗ It acts as a closed switch.

**Question Number : 63 Question Id : 7520766903 Question Type : MCQ**  
**Correct Marks : 1 Wrong Marks : 0**

What is the role of input capacitance in the transistor amplifying circuit?

**Options :**

1. ✗ To prevent input variation from reaching output

2. ✓ To prevent DC content in the input from reaching transistor

3. ✗ There isn't any role for input capacitance

4. ✗ To increase input impedance

**Question Number : 64 Question Id : 7520766904 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Given that  $R_1=20\text{k}\Omega$ ,  $C_1=2\text{nF}$ ,  $R_2=20\text{k}\Omega$ ,  $C_2=2\text{nF}$ , find the approximate resonant frequency of a Wein bridge oscillator.

**Options :**

1. ✓ 4kHz

2. ✗ 3kHz

3. ✗ 25kHz

4. ✗ 15kHz

Question Number : 65 Question Id : 7520766905 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which among the following can be used to detect the missing heart beat?


Options :

1. ✓ Mono-stable multivibrator
2. ✗ Astable multivibrator
3. ✗ Schmitt trigger
4. ✗ Filter

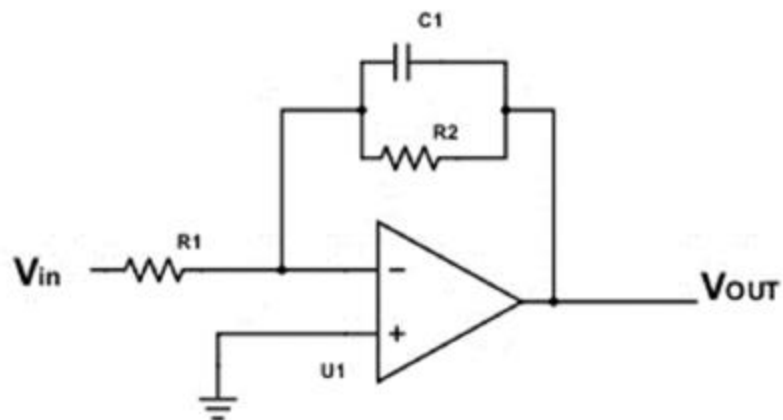Question Number : 66 Question Id : 7520766906 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a low pass filter as below, find the cut-off frequency for the following circuit. Given that  $R1=20k\Omega$ ,  $R2=25k\Omega$ ,  $C1=10\mu F$ .



Options :

1. ✘ 640 kHz
2. ✔ 637 Hz
3. ✘ 5.5 kHz
4. ✘ 200 Hz

**Question Number : 67 Question Id : 7520766907 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Which component is used to reduce ripples in a DC power supply?

**Options :**

1. ✘ Resistor
2. ✔ Filter
3. ✘ Transformer
4. ✘ Diode

Question Number : 68 Question Id : 7520766908 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following options comes under the non-saturated logic family?

Options :

1. ✓ Emitter – coupled Logic
2. ✗ High-Threshold Logic
3. ✗ Integrated – injection Logic
4. ✗ Diode – Transistor Logic

Question Number : 69 Question Id : 7520766909 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The result “ $X + XY = X$ ” follows which of these laws?

Options :

1. ✗ Consensus law
2. ✗ Distributive law


3. ✘ Duality law

4. ✔ Absorption law

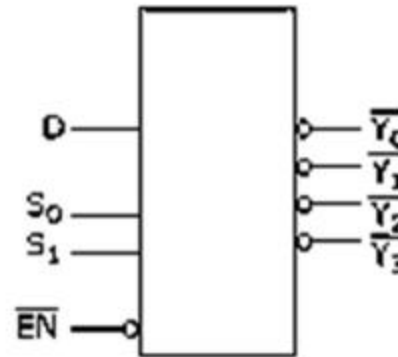Question Number : 70 Question Id : 7520766910 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The device shown here is most likely a \_\_\_\_\_.



Options :

1. ✘ Comparator

2. ✘ Multiplexer

3. ✘ Inverter

4. ✔ Demultiplexer

Question Number : 71 Question Id : 7520766911 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

How many select lines would be required for an 8-line-to-1-line multiplexer?

Options :

1. ✘ 2

2. ✘ 4

3. ✘ 8

4. ✔ 3

Question Number : 72 Question Id : 7520766912 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following is a register-indirect addressing mode instruction set?

Options :

1. ✘ LDA 2700H

2. ✘ ADI 36H

3. ✘ DAA

4. ✔ LDAX B

Question Number : 73 Question Id : 7520766913 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Find the ROC of  $x(t) = e^{-2t} u(t) + e^{-3t} u(t)$ .

Options :

1. ✘  $\sigma > 2$

2. ✘  $\sigma > 3$

3. ✔  $\sigma > -2$

4. ✘  $\sigma > -3$

Question Number : 74 Question Id : 7520766914 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following systems is memoryless?

Options :

1. ✘  $y(t) = x(2t) + x(t)$

2. ✔  $y(t) = x(t) + 2x(t)$

3. ✘  $y(t) = -x(t) + x(1-t)$

4. ✘  $y(t) = x(t) + 2x(t+2)$

**Question Number : 75 Question Id : 7520766915 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Find the convolution sum of sequences  $x_1[n] = (1, 2, 3)$  and  $x_2[n] = (2, 1, 4)$ .

**Options :**

1. ✔  $\{2, 5, 12, 11, 12\}$

2. ✘  $\{2, 12, 5, 11, 12\}$

3. ✘  $\{2, 11, 5, 12, 12\}$

4. ✘  $\{-2, 5, -12, 11, 12\}$

Question Number : 76 Question Id : 7520766916 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The total number of complex multiplications required to compute N point DFT by radix-2 FFT is?

Options :

1. ✓  $(N/2)\log_2 N$
2. ✗  $N\log_2 N$
3. ✗  $(N/2)\log N$
4. ✗  $(N/2)\log N/2$


Question Number : 77 Question Id : 7520766917 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The transfer function from D(s) to C(s)

is \_\_\_\_\_

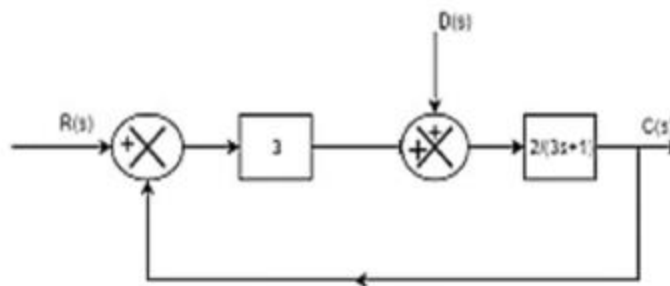Given  $G(s) = \frac{2}{3s+1}$  and  $H(s) = 3$



Options :

1. ✓  $2/3s+7$

2. ✗  $2/3s+1$

3. ✗  $6/3s+7$

4. ✗  $6/3s+7$

Question Number : 78 Question Id : 7520766918 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The greater the Gain Margin in the control system, the greater is its \_\_\_\_\_.

Options :

1. ✓ stability

2. ✗ response

3. ✗ profit

4. ✗ delay

Question Number : 79 Question Id : 7520766919 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The system with the open loop transfer function  $\frac{1}{s(1+s)}$  is:

Options :

1. ✘ Type 2 and order 1
2. ✘ Type 1 and order 1
3. ✘ Type 0 and order 0
4. ✔ Type 1 and order 2

Question Number : 80 Question Id : 7520766920 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

PD controller:

Options :

1. ✘ Decreases steady state error and improves stability
2. ✔ Rise time decreases

3. ✘ Transient response becomes poorer

4. ✘ Increases steady state error

**Question Number : 81 Question Id : 7520766921 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Calculate power in each sideband, if power of carrier wave is 176W and there is 60% modulation in amplitude modulated signal?

**Options :**

1. ✘ 13.36W

2. ✘ 52W

3. ✘ 67W

4. ✔ 15.84W

**Question Number : 82 Question Id : 7520766922 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

In flat top sampling scheme, \_\_\_\_\_ is kept constant after sampling.

**Options :**

1. ✓ amplitude
2. ✗ phase
3. ✗ frequency
4. ✗ time period

**Question Number : 83 Question Id : 7520766923 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

The matched filter is equivalent to which of the following?

**Options :**

1. ✓ A correlator
2. ✗ An envelope detector
3. ✗ A PLL
4. ✗ An equalizer

Question Number : 84 Question Id : 7520766924 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which access technique is primarily used in the Global System for Mobile communications (GSM)?

Options :

1. ✘ CDMA
2. ✔ TDMA
3. ✘ FDMA
4. ✘ WDMA

Question Number : 85 Question Id : 7520766925 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The cut off frequency of the dominant mode in a TE wave in the line having  $a$  and  $b$  as 2.5 cm and 1 cm respectively is,

Options :

1. ✘ 4.5 GHz

2. ✘ 5 GHz

3. ✘ 5.5 GHz

4. ✔ 6 GHz

**Question Number : 86 Question Id : 7520766926 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0**

Fresnel zone is also called as \_\_\_\_\_.

**Options :**

1. ✔ near Field

2. ✘ far Field

3. ✘ electrostatic Field

4. ✘ reactive Field

**Question Number : 87 Question Id : 7520766927 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0**

What does the parameter  $S_{11}$  represent in a two-port network?

Options :

1. ✘ Forward transmission coefficient
2. ✘ Reverse transmission coefficient.
3. ✔ Input reflection coefficient
4. ✘ Output reflection coefficient

Question Number : 88 Question Id : 7520766928 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

An amplifier without feedback has a voltage gain of 50, input resistance of  $1k\Omega$  and output resistance of  $2.5k\Omega$ . The input resistance of the current-shunt negative feedback amplifier using the above amplifier with a feedback factor of 0.2, is

Options :

1. ✔  $\frac{1}{11}k\Omega$

2. ✘  $\frac{1}{5}k\Omega$

3. ✘  $5k\Omega$

4. ✘  $11k\Omega$

Question Number : 89 Question Id : 7520766929 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

To double the drain current of an N-channel enhancement mode MOSFET biased in saturation \_\_\_\_\_.

Options :


1. ✘ channel length should be doubled
2. ✘ channel width should be halved
3. ✔ channel length should be halved
4. ✘ oxide thickness should be doubled

Question Number : 90 Question Id : 7520766930 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The MUX shown in fig is  $4 \times 1$  multiplexer.

The output Z is

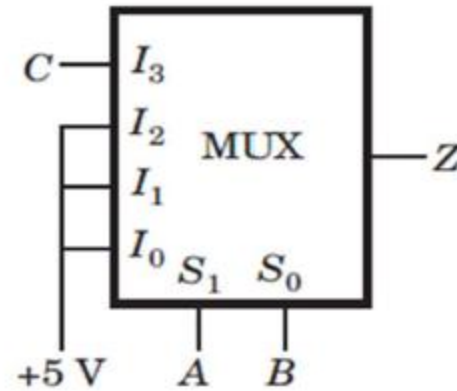


Options :

1. ✘  $ABC$
2. ✘  $A \oplus B \oplus C$
3. ✘  $A \cup B \cup C$
4. ✔  $A + B + C$

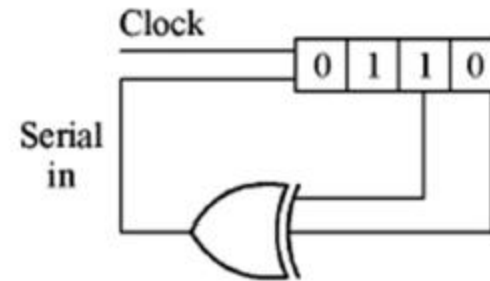Question Number : 91 Question Id : 7520766931 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The initial contents of the 4-bit serial-in-parallel out right-shift register shown in figure is 0110. After three clock pulse applied, the contents of the shift register will be



Options :

1. ✘ 0000
2. ✘ 0101
3. ✔ 1010
4. ✘ 1111

Question Number : 92 Question Id : 7520766932 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The contents of accumulator after the execution of following instruction will be

*MVI A, B7H*

*ORA A*

*RAL*

Options :

1. ✓  $6EH$

2. ✗  $6FH$


3. ✗  $EEH$

4. ✗  $EFH$

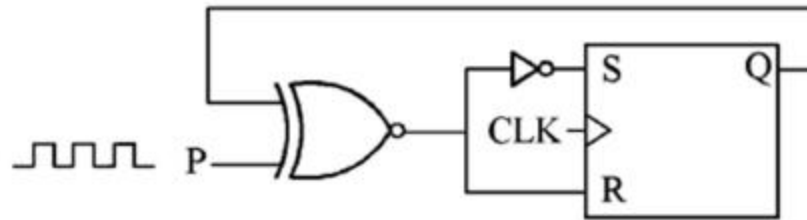Question Number : 93 Question Id : 7520766933 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Consider the circuit, the next state  $Q^+$  is



Options :

1. ✗  $PQ$

2. ✗  $P\bar{Q}$

3. ✓  $P\oplus Q$

4. ✘  $P \odot \bar{Q}$

Question Number : 94 Question Id : 7520766934 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A system is described by the differential equation  $\frac{d^2y(t)}{dt^2} + 6\frac{dy(t)}{dt} + 5y(t) = x(t)$

Impulse response of the system is

Options :

$$h(t) = \frac{1}{4}[e^{-2t} - e^{-3t}]u(t)$$

1. ✘

$$h(t) = [e^{-t} - e^{-5t}]u(t)$$

2. ✘

$$h(t) = \frac{1}{4}[e^{-t} - e^{-5t}]u(t)$$

3. ✔

$$h(t) = \frac{1}{4}[e^{-3t} - e^{2t}]u(t)$$

4. ✘

Question Number : 95 Question Id : 7520766935 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Fourier transform of a real valued time signal has \_\_\_\_\_.

Options :

1. ✘ odd symmetry
2. ✘ even symmetry
3. ✔ conjugate symmetry
4. ✘ no symmetry

Question Number : 96 Question Id : 7520766936 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Consider a causal LTI system with frequency response  $H(j\omega) = \frac{1}{j\omega+3}$ . This system

produces the output to an input  $x(t)$  as  $y(t) = e^{-3t}u(t) - e^{-4t}u(t)$ . The input

$x(t)$  is

Options :

1. ✘  $(2e^{-4t} - 3e^{-3t})u(t)$

2. ✓  $e^{-4t}u(t)$

3. ✗  $(3e^{-4t} - 2e^{-3t})u(t)$

4. ✗  $-e^{-4t}u(t)$

Question Number : 97 Question Id : 7520766937 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The convolution of two DT sequence is,

$$x(n) = \{1 \uparrow, 2, 0, 1\}$$

$$h(n) = \{2, 2, 3\}$$

Options :

1. ✘  $\{2 \uparrow, 4, 0, 2, 3, 6\}$

2. ✔  $\{2 \uparrow, 6, 7, 8, 2, 3\}$

3. ✘  $\{2, 6, 7, 8 \uparrow, 2, 3\}$

4. ✘  $\{2, 4, 0 \uparrow, 2, 3, 6\}$

Question Number : 98 Question Id : 7520766938 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The value of K for which the unity feedback system  $G(s) = \frac{K}{s(s+2)(s+4)}$  crosses

the imaginary axis is ,

Options :

1. ✘ 2

2. ✘ 4

3. ✘ 6

4. ✔ 48

Question Number : 99 Question Id : 7520766939 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A unity feedback second order system has  $G(s) = \frac{100}{s^2 + 10s + 100}$ . The 2% settling time is in second,

Options :

1. ✘ 0.4

2. ✔ 0.8


3. ✘ 1

4. ✘ 2

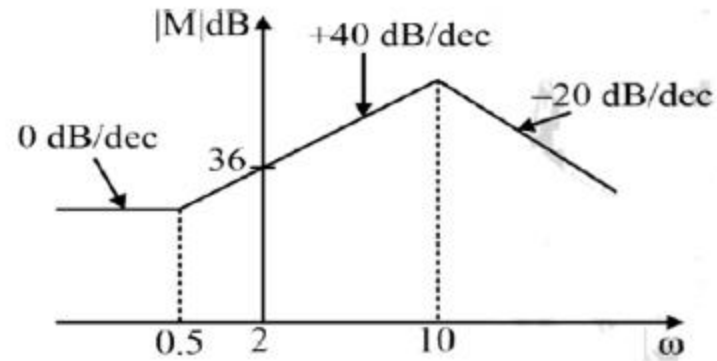Question Number : 100 Question Id : 7520766940 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

What is the transfer function for given bode plot shown in the figure?



Options :

1. ✘  $\frac{4(S + 0.5)^2}{(S + 10)^3}$


2. ✘  $\frac{4000(S + 0.5)^2}{(S + 10)^3}$

3. ✘  $\frac{160(S + 0.5)^2}{(S + 10)^3}$

4. ✔  $\frac{1600(S + 0.5)^2}{(S + 10)^3}$

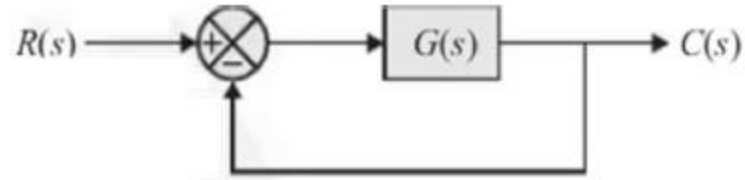Question Number : 101 Question Id : 7520766941 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

Consider the unity feedback system with  $G(S) = \frac{2}{s(s+1)(2s+1)}$ . what is the phase margin?



Options :

1. ✘  $\frac{1}{\sqrt{3}}$

2. ✘  $\frac{\sqrt{3}}{2}$


3. ✔  $\frac{1}{\sqrt{2}}$

4. ✘  $\sqrt{3}$

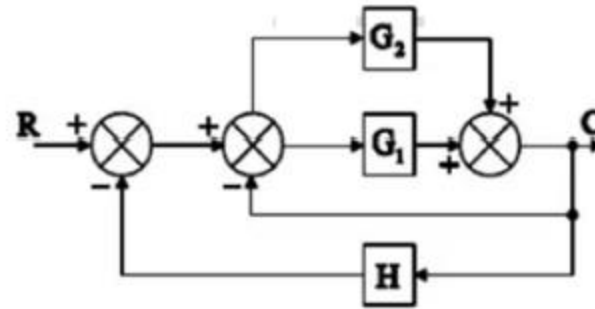Question Number : 102 Question Id : 7520766942 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Overall gain of the system shown in figure,



Options :

$$\frac{G_1 + G_2}{1 + G_1G_2 + G_1H + G_2H}$$

1. ✖

$$\frac{G_1G_2}{1 + G_1 + G_2 + G_1H + G_2H}$$

2. ✖

$$\frac{G_1G_2}{1 + G_1G_2 + G_1H + G_2H}$$

3. ✖

$$\frac{G_1 + G_2}{1 + G_1 + G_1 + G_1H + G_2H}$$

4. ✔

Question Number : 103 Question Id : 7520766943 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The carrier  $c(t) = A\cos 2\pi \times 10^6 t$  is angle modulated (PM or FM) by the signal

$m(t) = 2 \cos(4000\pi t)$ . The deviation constants are  $k_p = 3 \frac{\text{rad}}{\text{V}}$  &

$k_f = 3000 \text{ Hz/V}$ . The value of modulation indices  $\beta_f$  &  $\beta_p$  are

Options :

1. ✘ 6 & 3

2. ✘ 12 & 6

3. ✔ 3 & 6

4. ✘ 9 & 6

Question Number : 104 Question Id : 7520766944 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A binary channel with bit rate of 56kbps is available for uniform PCM voice transmission having signal bandwidth of 3.4kHz, signal to noise ratio in decibel

Options :

1. ✔ 58.8

2. ✘ 76.9

3. ✘ 98.6

4. ✘ 108.5

**Question Number : 105 Question Id : 7520766945 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

A binary signal is transmitted at 10kbps using NRZ signaling .find the minimum channel bandwidth required in KHz

**Options :**

1. ✘ 2.5

2. ✔ 5

3. ✘ 1.5

4. ✘ 20

**Question Number : 106 Question Id : 7520766946 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

In a DPSK system the input bit sequence is 1101, initial phase = 0. The transmitted phase sequence

Options :

1. ✓  $180^\circ, 0^\circ, 0^\circ, 180^\circ$
2. ✗  $0^\circ, 180^\circ, 180^\circ, 0^\circ$
3. ✗  $180^\circ, 180^\circ, 0^\circ, 0^\circ$
4. ✗  $180^\circ, 0^\circ, 0^\circ, 180^\circ$

Question Number : 107 Question Id : 7520766947 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

For electrostatic fields in charge free atmosphere, which one of the following is correct?

Options :

1. ✓  $\nabla \times E = 0 \text{ and } \nabla \cdot E = 0$
2. ✗  $\nabla \times E \neq 0 \text{ and } \nabla \cdot E = 0$

3. ✘  $\nabla \times E = 0$  and  $\nabla \cdot E \neq 0$

4. ✘  $\nabla \times E \neq 0$  and  $\nabla \cdot E \neq 0$

Question Number : 108 Question Id : 7520766948 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a non-magnetic medium electric field  $E = E_0 \cos \omega t$  is applied. If the permittivity of medium is  $\epsilon$  and the conductivity is  $\sigma$  then the ratio of the amplitudes of the conduction current density and displacement current density will be

Options :

1. ✘  $\mu_0 / \omega \epsilon$

2. ✔  $\sigma / \omega \epsilon$

3. ✘  $\sigma \mu_0 / \omega \epsilon$

4. ✘  $\omega \epsilon / \sigma$

Question Number : 109 Question Id : 7520766949 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If maximum and minimum voltage on a transmission line are 2V and 5V respectively, VSWR is

Options :

1. ✘ 0.5
2. ✔ 2
3. ✘ 1
4. ✘ 8

Question Number : 110 Question Id : 7520766950 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If a transmission line of characteristic impedance  $25 \Omega$  is to be matched to a load of  $100\Omega$ , then the characteristic impedance of the  $\lambda/4$  transmission line to be used is:

Options :

1. ✘  $70.71 \Omega$
2. ✔  $50 \Omega$

3. ✘  $100 \Omega$

4. ✘  $75 \Omega$

**Question Number : 111 Question Id : 7520766951 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Let  $A$  be a  $3 \times 3$  matrix with real entries such that  $\det(A) = 6$  and  $\text{trace}(A) = 0$ . If  $\det(A + I) = 0$ , where  $I$  is the  $3 \times 3$  identity matrix, then the eigenvalues of  $A$  are

**Options :**

1. ✘  $-1, 2, 3$

2. ✘  $-1, 2, -3$

3. ✘  $1, 2, -3$

4. ✔  $-1, -2, 3$

**Question Number : 112 Question Id : 7520766952 Question Type : MCQ**

**Correct Marks : 1 Wrong Marks : 0**

Consider the following system of equations

$$x - 2y + 3z = -1$$

$$x - 3y + 4z = 1$$

$$-2x + 4y - 6z = k$$

The value of  $k$  for which the system has infinitely many solutions is \_\_\_\_\_.

Options :

- 1. ✘ 0
- 2. ✘ 1
- 3. ✔ 2
- 4. ✘ -1

Question Number : 113 Question Id : 7520766953 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The value of the improper integral  $\int_{-\infty}^0 \frac{e^x}{e^{2x}+1} dx$  is equal to \_\_\_\_\_.

Options :

- 1. ✘ 0

2. ✘  $\frac{\pi}{2}$

3. ✔  $\frac{\pi}{4}$

4. ✘  $-\infty$

Question Number : 114 Question Id : 7520766954 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Suppose  $C$  is the closed curve defined as the circle  $x^2 + y^2 = 1$  with  $C$  oriented anti-clockwise. The value of the line integral  $\oint_C (x dy - y dx)$  is equal to \_\_\_\_\_.

Options :

1. ✘ 0

2. ✘  $\pi$

3. ✔  $2\pi$

4. ✘  $\frac{\pi}{2}$

Question Number : 115 Question Id : 7520766955 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The general solution of the differential equation  $x^2 \frac{d^2y}{dx^2} - 5x \frac{dy}{dx} + 13y = 0$  is \_\_\_\_\_.

Options :

1. ✖  $y = e^{3x}(C_1 \cos 2x + C_2 \sin 2x)$
2. ✖  $y = e^{3x}(C_1 \cos x + C_2 \sin x)$
3. ✔  $y = x^3(C_1 \cos(2 \ln x) + C_2 \sin(2 \ln x))$
4. ✖  $y = x^3(C_1 \cos(\ln x) + C_2 \sin(\ln x))$

Question Number : 116 Question Id : 7520766956 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Let  $S$  be the surface of the cube bounded by  $x = 0, x = 1, y = 0, y = 1, z = 0,$

$z = 1$ . The value of the surface integral  $\iint_S \vec{F} \cdot d\vec{s}$  of a vector field

$\vec{F} = 4xz\hat{i} - y^2\hat{j} + yz\hat{k}$  over the entire surface  $S$  of the cube, is \_\_\_\_\_.

Options :

1. ✖  $\frac{5}{2}$

2. ✘ 1

3. ✘  $\frac{1}{2}$

4. ✔  $\frac{3}{2}$

Question Number : 117 Question Id : 7520766957 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The value of the integral  $\int_C \frac{e^z}{z^3} dz$ , where  $C : |z| = 1$  is

Options :

1. ✘ 0

2. ✘ 1

3. ✔  $\pi i$

4. ✘  $2\pi i$

Question Number : 118 Question Id : 7520766958 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The coefficient of  $\frac{1}{z}$  in the Laurent's series expansion of the function  $f(z) = \frac{1}{z^2(1-z)}$  about  $z = 0$ , is \_\_\_\_\_.

Options :

1. ✘ -1
2. ✘ 0
3. ✔ 1
4. ✘ 2

Question Number : 119 Question Id : 7520766959 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Suppose that  $X$  has the density function  $f(x) = cx^2$  for  $0 \leq x \leq 1$  and  $f(x) = 0$  otherwise. What is  $P(0.1 \leq X \leq 0.5)$ ?

Options :

1. ✘  $\frac{1}{25}$

2. ✘  $\frac{6}{25}$

3. ✘  $\frac{4}{250}$

4. ✔  $\frac{31}{250}$

Question Number : 120 Question Id : 7520766960 Question Type : MCQ  
Correct Marks : 1 Wrong Marks : 0

Consider the function  $f(x) = x^3 - x - 1$  for finding the root of the equation  $f(x) = 0$ . If the initial approximation is  $x_0 = 1$ , then the next approximation  $x_1$  using the Newton–Raphson method is

Options :

1. ✘ 1.25

2. ✘ 1.75

3. ✔ 1.5

4. ✘ 2