

Andhra Pradesh State Council of Higher Education

Notations :

- 1.Options shown in green color and with ✓ icon are correct.
- 2.Options shown in red color and with ✖ icon are incorrect.

Question Paper Name :	Electrical Engineering 29th April 2026 Shift 2
Subject Name :	Electrical Engineering
Creation Date :	2026-04-29 16:37:35
Duration :	120
Number of Questions :	120
Total Marks :	120
Display Marks:	No
Change Font Color :	No
Change Background Color :	No
Change Theme :	No
Help Button :	No
Show Reports :	No
Show Progress Bar :	No

Electrical Engineering

Group Number :	1
Group Id :	75207657
Group Maximum Duration :	0
Group Minimum Duration :	120
Show Attended Group? :	No
Edit Attended Group? :	No
Break time :	0
Group Marks :	120

Electrical Engineering

Section Id :	75207657
Section Number :	1
Section type :	Online
Mandatory or Optional :	Mandatory
Number of Questions :	120
Number of Questions to be attempted :	120
Section Marks :	120
Section Negative Marks :	0
Maximum Instruction Time :	0
Sub-Section Number :	1
Sub-Section Id :	75207657
Question Shuffling Allowed :	Yes
Is Section Default? :	No

Question Number : 1 Question Id : 7520766721 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Minimum number of 2-input NAND gates required for implementing the logic

$F = AB + A' C$ is:

Options :

1. ✘ 3

2. ✔ 4

3. ✘ 5

4. ✘ 6

Question Number : 2 Question Id : 7520766722 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Universal gate is:

Options :

1. ✘ AND

2. ✘ OR

3. ✔ NAND

4. ✘ XOR

Question Number : 3 Question Id : 7520766723 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The MSB frequency of a 4-bit ripple counter with 16 MHz clock is

Options :

1. ✔ 1 MHz

2. ✘ 2 MHz

3. ✘ 4 MHz

4. ✘ 8 MHz

Question Number : 4 Question Id : 7520766724 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A JK flip-flop with $J=K=1$ behaves as:

Options :

1. ✘ Reset

2. ✘ Set

3. ✔ Toggle

4. ✘ Hold

Question Number : 5 Question Id : 7520766725 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Race-around occurs when:

Options :

1. ✔ Clock width small

2. ✘ Clock width $>$ propagation delay
3. ✘ Input zero
4. ✘ Output constant

Question Number : 6 Question Id : 7520766726 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

The number of Select lines required for a 16:1 MUX is

Options :

1. ✘ 2
2. ✘ 3
3. ✘ 4
4. ✔ 5

Question Number : 7 Question Id : 7520766727 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

The Karnaugh map is used for:

Options :

1. ✘ Timing
2. ✔ Simplification
3. ✘ Storage
4. ✘ Speed

Question Number : 8 Question Id : 7520766728 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A full adder can be built using:

Options :

1. ✘ One Half-Adder (HA)
2. ✔ Two HAs + OR
3. ✘ XOR only
4. ✘ Three HAs

Question Number : 9 Question Id : 7520766729 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A Decoder with n inputs has the following number of outputs:

Options :

1. ✘ n

2. ✔ 2^n

3. ✘ n^2

4. ✘ $\log n$

Question Number : 10 Question Id : 7520766730 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Setup time is the time:

Options :

1. ✘ After clock

2. ✔ Before the clock edge

3. ✘ During clock

4. ✘ Between outputs

Question Number : 11 Question Id : 7520766731 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Mealy output depends on:

Options :

1. ✘ State

2. ✔ State and Input

3. ✘ Input

4. ✘ Previous state

Question Number : 12 Question Id : 7520766732 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a moving coil instruments, the deflecting torque is proportional to:

Options :

1. ✘ I^2

2. ✔ I

3. ✘ V

4. ✘ Power

Question Number : 13 Question Id : 7520766733 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A Moving iron instrument measures:

Options :

1. ✘ DC only

2. ✘ AC only

3. ✔ AC and DC

4. ✘ Pulsating DC

Question Number : 14 Question Id : 7520766734 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In an analogue instrument, the Controlling torque is provided by:

Options :

1. ✘ Springs only

2. ✘ Damping

3. ✓ Spring or gravity

4. ✗ Gravity only

Question Number : 15 Question Id : 7520766735 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In measuring instruments, The Damping torque is used to:

Options :

1. ✗ Increase Sensitivity

2. ✓ Reduce Oscillations

3. ✗ Increase Deflection

4. ✗ Measure Current

Question Number : 16 Question Id : 7520766736 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a Voltmeter the sensitivity is given by:

Options :

1. ✓ Ω/V

2. ✘ V/Ω

3. ✘ A/V

4. ✘ W/V

Question Number : 17 Question Id : 7520766737 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

To minimize loading, the voltmeter should have:

Options :

1. ✘ Low Resistance

2. ✔ High Resistance

3. ✘ High Current

4. ✘ Low Voltage

Question Number : 18 Question Id : 7520766738 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A Permanent Magnet Moving Coil (PMMC) instrument can be used to measure:

Options :

1. ✓ DC quantities only
2. ✗ AC quantities only
3. ✗ Both AC and DC quantities
4. ✗ Only high-frequency AC

Question Number : 19 Question Id : 7520766739 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

Which bridge is best suited for the measurement of a high-quality factor (Q) inductor?

Options :

1. ✗ Maxwell's Bridge
2. ✓ Hay's Bridge
3. ✗ Anderson's Bridge
4. ✗ Schering Bridge

Question Number : 20 Question Id : 7520766740 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 100V voltmeter has an accuracy of $\pm 2\%$ of full-scale deflection (FSD). If it reads 50V, what is the limiting error?

Options :

1. ✘ $\pm 2\%$
2. ✘ $\pm 1\%$
3. ✔ $\pm 4\%$
4. ✘ $\pm 5\%$

Question Number : 21 Question Id : 7520766741 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The "Creeping" phenomenon occurs in which type of instrument?

Options :

1. ✘ PMMC Ammeter
2. ✔ Induction type Energy Meter

3. ✘ Digital Multimeter

4. ✘ Dynamometer Wattmeter

Question Number : 22 Question Id : 7520766742 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A digital voltmeter (DVM) with a $3\frac{1}{2}$ digit display can show a maximum count of:

Options :

1. ✘ 999

2. ✔ 1999

3. ✘ 3999

4. ✘ 9999

Question Number : 23 Question Id : 7520766743 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A Dynamometer-type instrument is primarily used as a "Transfer Instrument" because:

Options :

1. ✘ It has high sensitivity
2. ✘ It has a linear scale
3. ✔ It gives the same calibration for both AC and DC
4. ✘ It is very inexpensive

**Question Number : 24 Question Id : 7520766744 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0**

A Q-meter works on the principle of:

Options :

1. ✘ Mutual Induction
2. ✔ Series Resonance
3. ✘ Parallel Resonance
4. ✘ Piezoelectric effect

**Question Number : 25 Question Id : 7520766745 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0**

Which of the following is an "Active" transducer?

Options :

1. ✘ Strain Gauge
2. ✘ Thermistor
3. ✔ Thermocouple
4. ✘ LVDT

Question Number : 26 Question Id : 7520766746 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Lissajous patterns are used to measure:

Options :

1. ✘ Voltage and Current
2. ✘ Power and Energy
3. ✔ Frequency and Phase shift
4. ✘ Resistance and Inductance

Question Number : 27 Question Id : 7520766747 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The bridge used for the measurement of an unknown capacitance is:

Options :

1. ✘ Wheatstone Bridge
2. ✘ Wien Bridge
3. ✔ Schering Bridge
4. ✘ Kelvin Double Bridge

Question Number : 28 Question Id : 7520766748 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

For a Type-1 system, the steady-state error to a unit ramp input is:

Options :

1. ✘ Zero
2. ✔ $1/K_v$
3. ✘ Infinite
4. ✘ $1/(1+K_p)$

Question Number : 29 Question Id : 7520766749 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In the Routh-Hurwitz criterion, a system is stable if:

Options :

1. ✘ All elements in the first row are positive
2. ✔ All elements in the first column have the same sign
3. ✘ All roots are on the right-half plane
4. ✘ The determinant is zero

Question Number : 30 Question Id : 7520766750 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Root Locus always starts at the _____ and ends at the _____.

Options :

1. ✘ Zeros; Poles
2. ✔ Poles; Zeros
3. ✘ Origin; Infinity
4. ✘ Real axis; Imaginary axis

Question Number : 31 Question Id : 7520766751 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Boost converter output V_o is:

Options :

1. ✘ Less than V_{in}
2. ✘ Equal to V_{in}
3. ✔ Greater than V_{in}
4. ✘ Zero

Question Number : 32 Question Id : 7520766752 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A Gain Margin of 0 dB or a Phase Margin of 0 degrees indicates the system is:

Options :

1. ✘ Stable
2. ✘ Unstable
3. ✔ Marginally stable
4. ✘ Highly damped

Question Number : 33 Question Id : 7520766753 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Lead compensation is used primarily to:

Options :

1. ✘ Increase the steady-state accuracy
2. ✘ Reduce the bandwidth
3. ✔ Improve the transient response and increase speed
4. ✘ Eliminate noise

Question Number : 34 Question Id : 7520766754 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In State-Space representation, the "State Vector" consists of:

Options :

1. ✘ Only the input variables
2. ✔ The minimum set of variables that describe the system's future behavior
3. ✘ The output variables only
4. ✘ The coefficients of the transfer function

Question Number : 35 Question Id : 7520766755 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A system is "Controllable" if:

Options :

1. ✓ All states can be reached from an arbitrary initial state using an input
2. ✗ The output can be determined by observing the input
3. ✗ The eigenvalues are all negative
4. ✗ The transfer function has no zeros

Question Number : 36 Question Id : 7520766756 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The State Transition Matrix $\phi(t)$ is given by:

Options :

1. ✗ $\mathcal{L}^{-1}[sI - A]$
2. ✓ $\mathcal{L}^{-1}[(sI - A)^{-1}]$
3. ✗ $[sI - A]^{-1}$

4. ✘ e^{-At}

Question Number : 37 Question Id : 7520766757 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If the eigenvalues of the system matrix A are -2 and -5, the system is:

Options :

1. ✔ Stable

2. ✘ Unstable

3. ✘ Oscillatory

4. ✘ Critically stable

Question Number : 38 Question Id : 7520766758 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which plot is used to determine stability by looking at the encirclements of the point (-1, j0)?

Options :

1. ✘ Bode Plot

2. ✘ Root Locus
3. ✔ Nyquist Plot
4. ✘ Nichols Chart

Question Number : 39 Question Id : 7520766759 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

Adding a Zero to the transfer function generally:

Options :

1. ✔ Increases the overshoot and improves the speed of response
2. ✘ Decreases the overshoot
3. ✘ Makes the system unstable
4. ✘ Has no effect on the transient response

Question Number : 40 Question Id : 7520766760 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A diode current increases from 1 mA to 10 mA. Dynamic resistance changes by:

Options :

1. ✘ 10× increase
2. ✔ 10× decrease
3. ✘ Same
4. ✘ 100× decrease

Question Number : 41 Question Id : 7520766761 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A DC generator has flux doubled and speed halved. New EMF is

Options :

1. ✘ Doubled
2. ✘ Halved
3. ✔ Same
4. ✘ Zero

Question Number : 42 Question Id : 7520766762 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

An autotransformer converts 200V to 100V supplying same load. Copper saving is

Options :

1. ✘ 25%
2. ✔ 50%
3. ✘ 75%
4. ✘ 100%

Question Number : 43 Question Id : 7520766763 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A synchronous generator is over-excited and running in parallel with an identical generator at the same terminal voltage. The over-excited generator will:

Options :

1. ✘ Supply real power only
2. ✔ Supply reactive power only
3. ✘ Supply both real and reactive power

4. ✘ Absorb reactive power

Question Number : 44 Question Id : 7520766764 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 6-pulse HVDC rectifier produces which harmonics in AC line current?

Options :

1. ✔ 5th, 7th, 11th, 13th ...

2. ✘ 6th, 12th, 18th ...

3. ✘ 3rd, 9th, 15th ...

4. ✘ Only 1st

Question Number : 45 Question Id : 7520766765 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 12-pulse HVDC link: line voltage = 220 kV (LL), $\alpha = 30^\circ$. Approximate DC voltage:

Options :

1. ✘ 220 kV

2. ✘ 238 kV

3. ✓ 325 kV

4. ✗ 200 kV

Question Number : 46 Question Id : 7520766766 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

An overcurrent relay operates at 1.2pu for 2 s. Fault current = 3pu. What is the expected operation time if relay is inverse-time type?

Options :

1. ✓ <2s

2. ✗ 2s

3. ✗ >2s

4. ✗ Depends on system voltage

Question Number : 47 Question Id : 7520766767 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If $A^2 = 0$, then:

Options :

1. ✘ $e^{At} = I$

2. ✔ $e^{At} = I + At$

3. ✘ $e^{At} = At$

4. ✘ Infinite series required

Question Number : 48 Question Id : 7520766768 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

An AC voltage controller reduces the RMS voltage across a resistive load to 0.5 of its original value. What is the reduction in power?

Options :

1. ✘ 50%

2. ✔ 75%

3. ✘ 25%

4. ✘ No change

Question Number : 49 Question Id : 7520766769 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The property of state transition matrix , $\phi(t_1 + t_2) =$

Options :

1. ✘ $\phi(t_1) + \phi(t_2)$
2. ✔ $\phi(t_1) * \phi(t_2)$
3. ✘ $\phi(t_1) - \phi(t_2)$
4. ✘ $\phi(t_1)/\phi(t_2)$

Question Number : 50 Question Id : 7520766770 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a connected electrical network graph, which statement about Kirchhoff's Current Law (KCL) is most accurate?

Options :

1. ✘ KCL is derived from Faraday's law of electromagnetic induction and applies only to mesh analysis.
2. ✘ KCL is applicable only to resistive networks under steady state DC conditions and is not valid for AC circuits.

3. ✓ KCL is valid only for networks consisting of linear and time-invariant elements.

KCL is based on the principle of conservation of charge and states that the algebraic sum of currents at a node is zero

4. ✘

Question Number : 51 Question Id : 7520766771 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A series RL circuit consists of a resistor $R=10\ \Omega$ and an inductor $L=1\text{H}$, connected to a DC voltage source of $V=20\text{ V}$. The switch is closed at $t=0$, and the initial current is zero. Determine the expression for the current $i(t)$ through the inductor for $t>0$, assuming ideal components.

Options :

1. ✘ $i(t)=2e^{-10t}\text{ A}$

2. ✘ $i(t)=2(1-e^{-0.1t})\text{ A}$

3. ✓ $i(t)=2(1-e^{-10t})\text{ A}$

4. ✘ $i(t)=2e^{-0.1t}\text{ A}$

Question Number : 52 Question Id : 7520766772 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A series RLC circuit has $R = 10 \Omega$, $L = 1 \text{ H}$, $C = 100 \mu\text{F}$. At resonance, the impedance is:

Options :

1. ✘ 0Ω
2. ✔ 10Ω
3. ✘ 100Ω
4. ✘ Depends on frequency

Question Number : 53 Question Id : 7520766773 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In an induction motor, maximum torque occurs when:

Options :

1. ✘ $R_2 = X_2$
2. ✘ $R_2 = sX_2$

3. ✘ $\frac{R_2}{s} = X_2$

4. ✔ $\frac{R_2}{X_2} = s_m$

Question Number : 54 Question Id : 7520766774 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A balanced three-phase, star-connected source with a line-to-line RMS voltage of 400V supplies a balanced star-connected load. Each phase of the load has a resistance of 20Ω . Neglect the line impedance. Calculate the total active power consumed by the load.

Options :

1. ✘ 6 kW

2. ✔ 4 kW

3. ✘ 12 kW

4. ✘ 8 kW

Question Number : 55 Question Id : 7520766775 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a Capacitor-start motor, main winding current is 2.0 pu, auxiliary winding current is 2.0 pu and the phase difference is 90° . Then the starting torque is,

Options :

1. ✘ 2.0 pu

2. ✔ 4.0 pu

3. ✘ 6.0 pu

4. ✘ 8.0 pu

Question Number : 56 Question Id : 7520766776 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A stepper motor with a step angle 1.8° requires _____ steps per one revolution.

Options :

1. ✘ 180

2. ✔ 200

3. ✘ 360

4. ✘ 100

Question Number : 57 Question Id : 7520766777 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which of the following is true about hunting in synchronous machines?

Options :

1. ✘ Occurs at low speed only
2. ✔ Occurs when mechanical load fluctuates
3. ✘ Is due to sudden change in field current
4. ✘ Is due to interaction between rotor inertia and synchronizing torque


Question Number : 58 Question Id : 7520766778 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A series RL circuit has $V = 10\text{ V}$, $R = 5\ \Omega$,

$L = 2\text{ H}$. With $i(t) = (V/R)(1 - e^{(-t/\tau)})$,

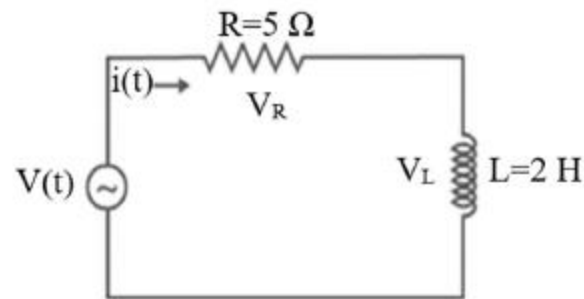$\tau = L/R$. Find i at $t = 0.5\text{ s}$.




Options :

1. ✘ 1.26 A
2. ✔ 1.428A
3. ✘ 2.00 A
4. ✘ 0.95 A

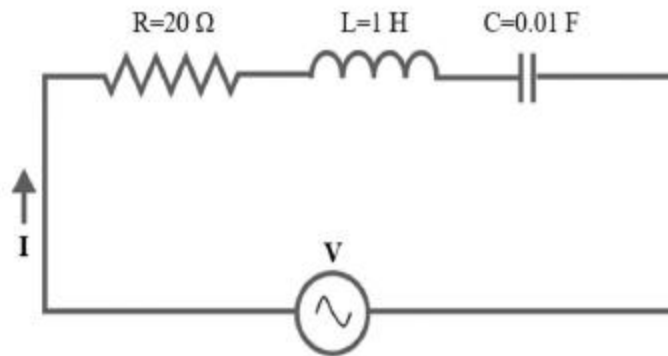Question Number : 59 Question Id : 7520766779 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A series RLC circuit has $R=20\ \Omega$, $L=1\ \text{H}$,
 $C=0.01\ \text{F}$.

Using $\zeta = R/(2\sqrt{L/C})$, the response is:



Options :

1. ✘ Underdamped
2. ✔ Critically damped


3. ✘ Overdamped

4. ✘ Sustained oscillations

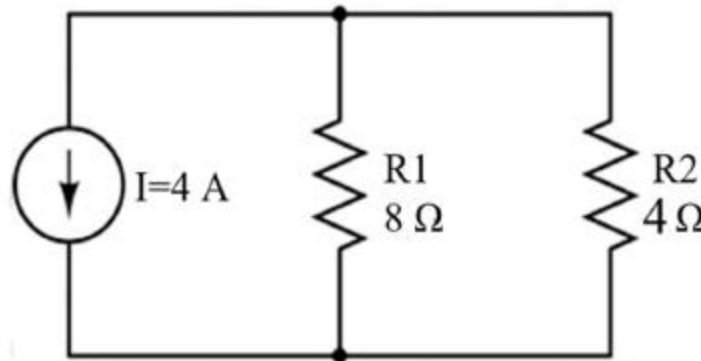Question Number : 60 Question Id : 7520766780 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 4 A current source feeds $8\ \Omega$
and $4\ \Omega$ in parallel. Power in $8\ \Omega$
is:



Options :

1. ✘ 32 W

2. ✘ 16 W


3. ✔ 14.22 W

4. ✘ 10.67 W

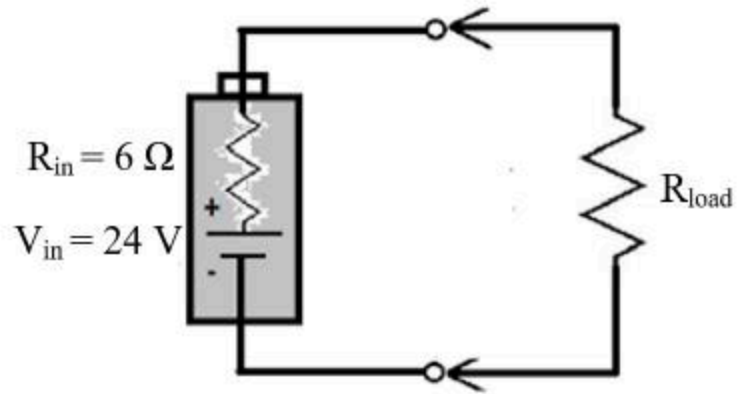Question Number : 61 Question Id : 7520766781 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 24 V source with internal resistance $6\ \Omega$ feeds a load. Maximum power to load is:



Options :

1. ✓ 24 W
2. ✗ 48 W
3. ✗ 36 W
4. ✗ 12 W

Question Number : 62 Question Id : 7520766782 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

$v(t) = 50\sqrt{2} \sin(\omega t)$ is applied to $Z = 3 + j4\ \Omega$. Average power is:

Options :

1. ✘ 200 W
2. ✘ 250 W
3. ✔ 300 W
4. ✘ 400 W

Question Number : 63 Question Id : 7520766783 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

With dependent sources, Thevenin's resistance is found by:

Options :

1. ✘ Open-circuit method
2. ✘ Short-circuit method
3. ✔ Applying a test source (V/I)
4. ✘ Ignoring sources

Question Number : 64 Question Id : 7520766784 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Maximum power transfer in an AC network occurs when:

Options :

1. ✘ $R_L = R_S$

2. ✔ $Z_L = Z_S^*$

3. ✘ $Z_L = Z_S$

4. ✘ $R_L = 0$

Question Number : 65 Question Id : 7520766785 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Newton–Raphson method is preferred because it,

Options :

1. ✘ is simplest

2. ✔ has Quadratic Convergence

3. ✘ uses fewer equations

4. ✘ avoids iteration

Question Number : 66 Question Id : 7520766786 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a per-unit system, the base impedance (Z_{base}) is defined as:

Options :

1. ✘ $V_{base} \times I_{base}$

2. ✔ V_{base}/I_{base}

3. ✘ I_{base}/V_{base}

4. ✘ $V_{base}^2 \times P_{base}$

Question Number : 67 Question Id : 7520766787 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Swing Equation describes the relationship between:

Options :

1. ✘ Voltage and Current

2. ✓ Power Angle and Rotor Dynamics
3. ✗ Fault Current and Time
4. ✗ Real Power and Reactive Power

Question Number : 68 Question Id : 7520766788 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a Load Flow study, which parameters are known at a PQ (Load) bus?

Options :

1. ✗ P and V
2. ✗ V and δ
3. ✓ P and Q
4. ✗ Q and δ

Question Number : 69 Question Id : 7520766789 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The "Equal Area Criterion" is used to determine:

Options :

1. ✘ Economic Dispatch
2. ✘ Fault Current Magnitude
3. ✔ Transient Stability Limits
4. ✘ Transmission Line Losses

Question Number : 70 Question Id : 7520766790 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If the supply frequency increases, the Skin Effect in a conductor:

Options :

1. ✔ Increases
2. ✘ Decreases
3. ✘ Remains the same
4. ✘ Becomes zero

Question Number : 71 Question Id : 7520766791 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 100 MVA, 11 kV generator has a reactance of 0.2 pu. What is the reactance in ohms?

Options :

1. ✓ 0.242 Ω
2. ✗ 2.42 Ω
3. ✗ 24.2 Ω
4. ✗ 1.21 Ω

Question Number : 72 Question Id : 7520766792 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Differential protection is primarily used for:

Options :

1. ✗ Long Transmission Lines
2. ✓ Transformers and Generators
3. ✗ Distribution Feeders
4. ✗ Lightning Protection

Question Number : 73 Question Id : 7520766793 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In Economic Load Dispatch, the most efficient operation occurs when:

Options :

1. ✘ All units operate at max capacity.
2. ✔ Incremental fuel costs of all units are equal.
3. ✘ Total fuel consumption is maximized.
4. ✘ All units carry equal loads.

Question Number : 74 Question Id : 7520766794 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

What is the primary purpose of a FACTS device like a STATCOM?

Options :

1. ✘ To break circuit arcs.
2. ✔ To provide fast-acting reactive power compensation.
3. ✘ To measure harmonic distortion.
4. ✘ To convert AC to DC

Question Number : 75 Question Id : 7520766795 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

HVDC transmission is preferred over HVAC for very long distances because:

Options :

1. ✘ DC equipment is cheaper.
2. ✔ There are no charging current losses or skin effect.
3. ✘ It doesn't require transformers.
4. ✘ It is easier to tap off power.

Question Number : 76 Question Id : 7520766796 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which relay is most affected by power swings?

Options :

1. ✔ Mho Relay
2. ✘ Differential Relay
3. ✘ Over-current Relay

4. ✘ Buchholz Relay

Question Number : 77 Question Id : 7520766797 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The "Corona Effect" in a transmission line is most likely to occur during

Options :

1. ✘ High-voltage transmission in fair weather
2. ✘ Low-voltage transmission in humid weather
3. ✔ High-voltage transmission in rainy or foggy weather
4. ✘ Low-voltage transmission in dry weather

Question Number : 78 Question Id : 7520766798 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A symmetrical 3-phase fault occurs at a bus. If the pre-fault voltage is 1.0pu and the Thevenin impedance is $j0.2\text{pu}$, the fault current in per-unit is:

Options :

1. ✘ 0.2pu

2. ✘ 2.0pu

3. ✔ 5.0pu

4. ✘ 10.0pu

Question Number : 79 Question Id : 7520766799 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If a transmission line carries 100 MW at unity power factor, the reactive power is:

Options :

1. ✔ 0 MVAR

2. ✘ 50 MVAR

3. ✘ 1000 MVAR

4. ✘ 10 MVAR

Question Number : 80 Question Id : 7520766800 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a single-phase transformer, the core is laminated primarily to reduce:

Options :

1. ✘ Copper loss
2. ✘ Hysteresis loss
3. ✔ Eddy current loss
4. ✘ Friction loss

Question Number : 81 Question Id : 7520766801 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 200/100 V transformer has a primary resistance of 0.1Ω . What is this resistance when referred to the secondary side?

Options :

1. ✘ 0.4Ω
2. ✘ 0.2Ω
3. ✘ 0.05Ω
4. ✔ 0.025Ω

Question Number : 82 Question Id : 7520766802 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

For two three-phase transformers to operate in parallel, which of these is an absolute requirement?

Options :

1. ✘ Same KVA rating
2. ✘ Same cooling method
3. ✔ Same phase sequence
4. ✘ Same percentage impedance

Question Number : 83 Question Id : 7520766803 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

An auto-transformer is most efficient when the transformation ratio ($K = V_2/V_1$)

is:

Options :

1. ✘ Near zero
2. ✔ Near unity (1.0)

3. ✘ Exactly 0.5
4. ✘ Greater than 10

Question Number : 84 Question Id : 7520766804 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

In a DC Machine, the function of the commutator is to:
Options :

1. ✘ Convert AC to DC in a generator
2. ✘ Convert DC to AC in a motor
3. ✔ Convert AC to DC in a generator and DC to AC in a motor
4. ✘ Increase the speed of the machine

Question Number : 85 Question Id : 7520766805 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

The effect of "Armature Reaction" in a DC generator mainly results in:
Options :

1. ✔ Cross-magnetization and demagnetization

2. ✘ Increased terminal voltage
3. ✘ Improved commutation
4. ✘ Reduction in mechanical friction

Question Number : 86 Question Id : 7520766806 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A 4-pole, 50 Hz induction motor has a synchronous speed of:

Options :

1. ✘ 1000 rpm
2. ✔ 1500 rpm
3. ✘ 3000 rpm
4. ✘ 750 rpm

Question Number : 87 Question Id : 7520766807 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If the air gap of an induction motor is increased, then,

Options :

1. ✘ Efficiency will increase
2. ✔ Magnetizing current will increase
3. ✘ Power factor will improve
4. ✘ Speed will increase

Question Number : 88 Question Id : 7520766808 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

The starting torque of a capacitor-start single-phase induction motor is:

Options :

1. ✘ Zero
2. ✘ Low
3. ✔ High
4. ✘ Same as a shaded-pole motor

Question Number : 89 Question Id : 7520766809 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A synchronous motor can be used for power factor correction when it is:

Options :

1. ✘ Under-excited only
2. ✔ Over-excited only
3. ✘ Operating at no load only
4. ✘ Both Over-excited and Operating at no load

Question Number : 90 Question Id : 7520766810 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

In a synchronous generator, "Voltage Regulation" is negative when the load is:

Options :

1. ✘ Purely resistive
2. ✘ Inductive (Lagging)
3. ✔ Capacitive (Leading)

4. ✘ Unity power factor

Question Number : 91 Question Id : 7520766811 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The "Hunting" in synchronous machines can be prevented by using:

Options :

1. ✘ Slip rings

2. ✔ Damper windings

3. ✘ Carbon brushes

4. ✘ Compensating windings

Question Number : 92 Question Id : 7520766812 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A Servo Motor differs from a standard motor because it:

Options :

1. ✘ Cannot be used for AC

2. ✘ Operates only at very high speeds

3. ✓ Features a feedback mechanism for precise control
4. ✗ Does not have a rotor

Question Number : 93 Question Id : 7520766813 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

What happens if the field winding of a running DC Shunt motor suddenly opens?

Options :

1. ✗ The motor stops immediately
2. ✗ The motor speed remains constant
3. ✓ The motor attains dangerously high speed
4. ✗ The motor starts running in reverse

Question Number : 94 Question Id : 7520766814 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A signal $x(t) = \cos(2\pi t) + \sin(3\pi t)$ is:

Options :

1. ✓ Periodic only

2. ✘ Aperiodic only
3. ✘ Both periodic and even
4. ✘ Neither periodic nor odd

Question Number : 95 Question Id : 7520766815 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If $x[n] = u[n]$ and $h[n] = u[n - 2]$, find the value of $y[5]$.

Options :

1. ✘ 3
2. ✔ 4
3. ✘ 5
4. ✘ 6

Question Number : 96 Question Id : 7520766816 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If energy of $x(t) = e^{-2t}u(t)$ is 0.25, find a :

Options :

1. ✘ 1

2. ✔ 3

3. ✘ 2

4. ✘ $\frac{1}{4}$

Question Number : 97 Question Id : 7520766817 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If $x(t) \leftrightarrow X(\omega)$, then FT of $tx(t)$ is:

Options :

1. ✔ $j \frac{dX(\omega)}{d\omega}$

2. ✘ $-j \frac{dX(\omega)}{d\omega}$

3. ✘ $jX(\omega)$

4. ✘ $\frac{X(\omega)}{\omega}$

Question Number : 98 Question Id : 7520766818 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

A signal contains frequencies up to 4π rad/sec. Minimum sampling frequency is

Options :

1. ✘ 4π

2. ✔ 8π

3. ✘ 2π

4. ✘ 16π

Question Number : 99 Question Id : 7520766819 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Given $X(s) = \frac{1}{s+2}$, ROC: $Re(s) > -2$. Signal is:

Options :

1. ✔ $e^{-2t}u(t)$

2. ✘ $-e^{-2t}u(-t)$

3. ✘ $e^{2t}u(t)$

4. ✘ $e^{-2t}u(-t)$

Question Number : 100 Question Id : 7520766820 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

Find the z-transform of $x[n] = \delta[n] + \delta[n + 1]$:

Options :

1. ✘ $1 + z^{-1}$

2. ✘ $z + 1$

3. ✔ $1 + z$

4. ✘ z^{-1}

Question Number : 101 Question Id : 7520766821 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If the Impulse response is $h[n] = (0.5)^n u(n)$ then, the system is

Options :

1. ✘ unstable
2. ✔ stable
3. ✘ marginally stable
4. ✘ time-varying

Question Number : 102 Question Id : 7520766822 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The z-transform of $a^n u(n)$ is:

Options :

1. ✔ $\frac{z}{z - a}$
2. ✘ $\frac{1}{1 - az}$

3. ✘ $\frac{1}{z - a}$

4. ✘ $\frac{1}{1 + az}$

Question Number : 103 Question Id : 7520766823 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

Which of the following system is linear?

Options :

1. ✘ $y(t) = x^2(t)$

2. ✘ $y(t) = 3x(t) + 2$

3. ✔ $y(t) = x(t) + x(t - 1)$

4. ✘ $y(t) = \sin(x(t))$

Question Number : 104 Question Id : 7520766824 Question Type : MCQ
Correct Marks : 1 Wrong Marks : 0

A band limited signal with $f_{max} = 5Hz$ is sampled at 8kHz. The result is:

Options :

1. ✘ Perfect reconstruction
2. ✔ Aliasing
3. ✘ No distortion
4. ✘ Infinite bandwidth

Question Number : 105 Question Id : 7520766825 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Aliasing occurs when,

Options :

1. ✘ Sampling rate is higher than Nyquist rate
2. ✔ Sampling rate is lower than Nyquist rate
3. ✘ Signal is periodic
4. ✘ Signal is even

Question Number : 106 Question Id : 7520766826 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The SCR triggers when:

Options :

1. ✓ Gate pulse with forward bias
2. ✗ Reverse voltage
3. ✗ Temperature rises
4. ✗ Current zero

Question Number : 107 Question Id : 7520766827 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

3 – ϕ fully controlled rectifier $V_{avg} \propto$:

Options :

1. ✗ $(3V_m/\pi)\cos\alpha$
2. ✓ $(3\sqrt{3}V_m/\pi)\cos\alpha$

3. ✘ $(6V_m/\pi)\cos\alpha$

4. ✘ $(V_m/\pi)\cos\alpha$

Question Number : 108 Question Id : 7520766828 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The FIFO structure represents a:

Options :

1. ✘ Stack

2. ✔ Queue

3. ✘ Tree

4. ✘ Graph

Question Number : 109 Question Id : 7520766829 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Output of the statement `int x = 5; printf("%d,x ++)` is;

Options :

1. ✓ 5

2. ✗ 6

3. ✗ 0

4. ✗ Error

Question Number : 110 Question Id : 7520766830 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The Advantages of Renewable energy sources are:

Options :

1. ✗ High cost

2. ✗ Pollution

3. ✓ Sustainability

4. ✗ Low efficiency

Question Number : 111 Question Id : 7520766831 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Consider the following system of equations

$$x - 2y + 3z = -1$$

$$x - 3y + 4z = 1$$

$$-2x + 4y - 6z = k$$

The value of k for which the system has infinitely many solutions is _____

Options :

1. ✘ 0

2. ✘ 1

3. ✔ 2

4. ✘ -1

Question Number : 112 Question Id : 7520766832 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If a 2×2 matrix A has eigenvalues 1 and 4 with the corresponding

eigenvectors $\begin{pmatrix} 1 \\ -1 \end{pmatrix}$ and $\begin{pmatrix} 2 \\ 1 \end{pmatrix}$, respectively, then A is _____

Options :

1. ✘ $\begin{pmatrix} -4 & -8 \\ 5 & 9 \end{pmatrix}$

2. ✘ $\begin{pmatrix} 9 & -8 \\ 5 & -4 \end{pmatrix}$

3. ✘ $\begin{pmatrix} 2 & 2 \\ 1 & 3 \end{pmatrix}$

4. ✔ $\begin{pmatrix} 3 & 2 \\ 1 & 2 \end{pmatrix}$

Question Number : 113 Question Id : 7520766833 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Let $f(x)$ be a differentiable function at $x = a$ with $f'(a) = 4$ and $f(a) = 8$.

Then,

$$\lim_{x \rightarrow a} \frac{xf(a) - af(x)}{x - a} = \underline{\hspace{2cm}}$$

Options :

1. ✘ $4(1 - 2a)$

2. ✘ $4(2a - 1)$

3. ✔ $4(2 - a)$

4. ✘ $4(a - 2)$

Question Number : 114 Question Id : 7520766834 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The directional derivative of $f(x, y) = x^2 + 3xy$ at the point (1,2) in the direction of the vector $3\hat{i} + 4\hat{j}$ is

Options :

1. ✘ $\frac{22}{5}$

2. ✘ $\frac{24}{5}$

3. ✘ $\frac{12}{5}$

4. ✔ $\frac{36}{5}$

Question Number : 115 Question Id : 7520766835 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

If $y(x)$ satisfies the differential equation $(\sin x) \frac{dy}{dx} + y \cos x - 1 = 0$ subject to the condition $y\left(\frac{\pi}{2}\right) = 0$, then $y\left(\frac{\pi}{6}\right) = \underline{\hspace{2cm}}$

Options :

1. ✘ $\frac{\pi}{3}$

2. ✔ $\frac{-2\pi}{3}$

3. ✘ $\frac{-\pi}{6}$

4. ✘ $\frac{-\pi}{3}$

Question Number : 116 Question Id : 7520766836 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Which one of the following functions is analytic over the entire complex plane?

Options :

1. ✘ $e^{\frac{1}{z}}$

2. ✓ $\cos z$

3. ✗ $\frac{2}{1-z}$

4. ✗ $\ln z$

Question Number : 117 Question Id : 7520766837 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Two dice are thrown. Let A be the event that the sum of the points on the faces is 9. Let B be the event that at least one of them is 6. Then, $(\bar{A} \cup \bar{B}) = \underline{\hspace{2cm}}$, where \bar{A} and \bar{B} are the complementary events of A and B , respectively.

Options :

1. ✓ $\frac{17}{18}$

2. ✗ $\frac{1}{18}$

3. ✗ $\frac{1}{9}$

4. ✘ $\frac{8}{9}$

Question Number : 118 Question Id : 7520766838 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Let C be the circle $|z| = \frac{3}{2}$ in the complex plane that is oriented in the counter clockwise direction. The value of a for which $\int_C \left(\frac{z+1}{z^2-3z+2} + \frac{a}{z-1} \right) dz = 0$ is _____

Options :

1. ✘ 1

2. ✘ -1

3. ✔ 2

4. ✘ -2

Question Number : 119 Question Id : 7520766839 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

The regression lines of a sample are $x + 6y = 6$ and $3x + 2y = 10$. Then the sample means and the correlation coefficient are _____

Options :

1. ✓ $\bar{x} = 3, \bar{y} = \frac{1}{2}, r = -\frac{1}{3}$

2. ✗ $\bar{x} = 3, \bar{y} = \frac{1}{2}, r = \frac{1}{3}$

3. ✗ $\bar{x} = \frac{1}{2}, \bar{y} = 3, r = -\frac{1}{3}$

4. ✗ $\bar{x} = \frac{1}{2}, \bar{y} = 3, r = \frac{1}{3}$

Question Number : 120 Question Id : 7520766840 Question Type : MCQ

Correct Marks : 1 Wrong Marks : 0

Consider the fixed-point iteration $x_{k+1} = g(x_k)$ with $g(x) = \frac{x}{3} + \frac{4}{3x}$. Which root-finding

problem is this equivalent to?

Options :

1. ✗ $x - \frac{1}{3} + \frac{4}{3x^2} = 0$

2. ✖ $\frac{x}{3} + \frac{4}{3x} = 0$

3. ✖ $\frac{1}{3} - \frac{4}{3x^2} = 0$

4. ✔ $x^2 - 2 = 0$